


# 0111

## *A Single Cycle CPU*

ENGR 3410 - Computer Architecture  
Fall 2010

### Datapath & Control

- Readings 4.1 – 4.4

 

- Datapath: System for performing operations on data, plus memory access.
- Control: Control the datapath in response to instructions.


## Simple CPU

Develop complete CPU for subset of instruction set


Memory: lw, sw

Branch: beq


Arithmetic: addi

 

Arithmetic: add, sub

 


Jump: j

 

Most other instructions similar


## Execution Cycle

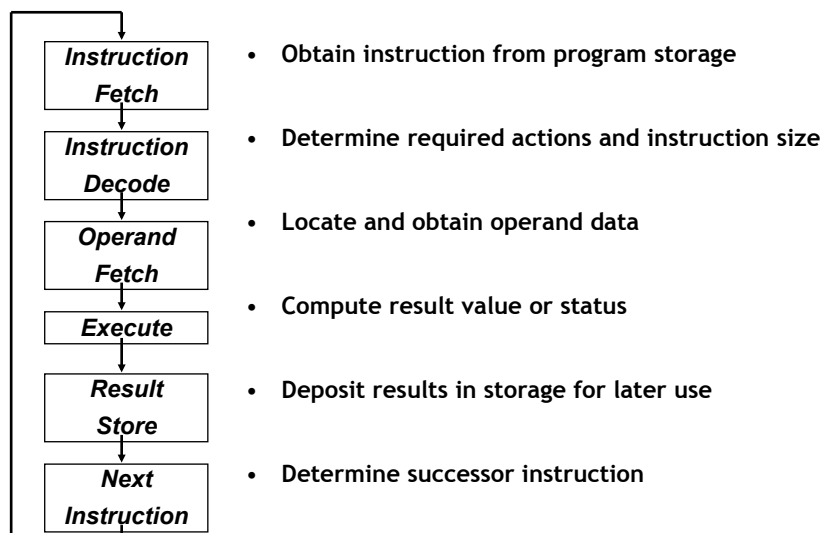

## Processor Overview
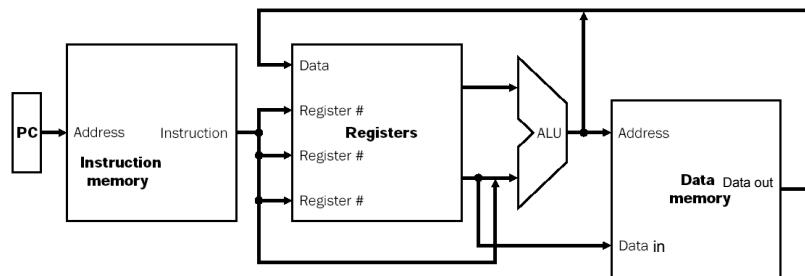
### Overall Dataflow

PC fetches instructions  
Instructions select operand registers, ALU immediate values  
ALU computes values  
Load/Store addresses computed in ALU  
Result goes to register file or Data memory



## Processor Design

### Convert instructions to Register Transfer Level (RTL) specification

```
Instruction = Memory[PC];  
PC = PC + 4;
```

RTL specifies required interconnection of units and specifies semantics

Control designed to achieve given paths for each instruction

## Instruction Fetch

```
Instruction = Mem[PC];    // Fetch Instruction  
PC = PC + 4;              // Increment PC (32bit)
```

## Instruction Fetch

```
Instruction = Mem[PC];    // Fetch Instruction  
PC = PC + 4;              // Increment PC (32bit)
```



## Add/Subtract RTL

**Add instruction:** `add rd, rs, rt`

`Instruction = Mem[PC];`

`Reg[rd] = Reg[rs] + Reg[rt];`


`PC = PC + 4;`

**Subtract instruction:** `sub rd, rs, rt`

`Instruction = Mem[PC];`

`Reg[rd] = Reg[rs] - Reg[rt];`


`PC = PC + 4;`

 

R-format

## Datapath for Reg/Reg Ops



`Reg[rd] = Reg[rs] op Reg[rt];`

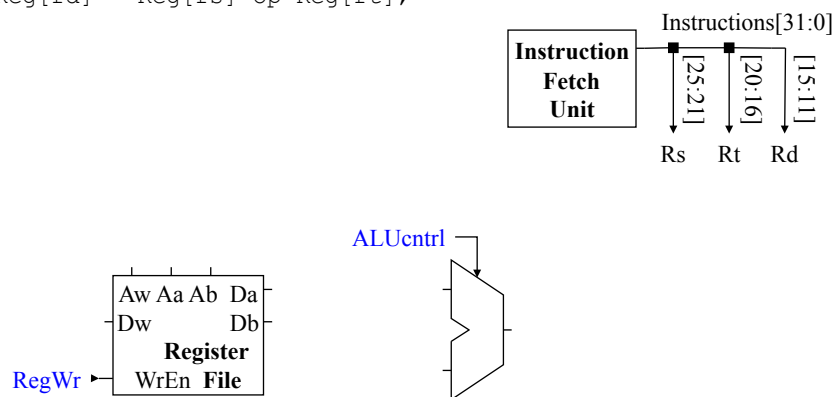
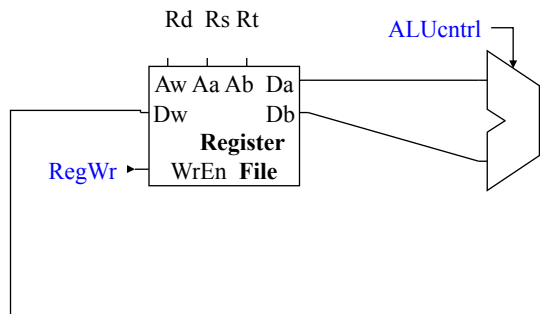 
## Datapath for Reg/Reg Ops

$\text{Reg}[\text{rd}] = \text{Reg}[\text{rs}] \text{ op } \text{Reg}[\text{rt}];$

ALUctrl based on Function, OP  
RegWr true when doing such an OP




## Add Immediate RTL

Add immediate instruction: `addi rt, rs, imm`

$\text{Instruction} = \text{Mem}[\text{PC}];$

$\text{Reg}[\text{rt}] = \text{Reg}[\text{rs}] + \text{SignExtend}(\text{imm});$


$\text{PC} = \text{PC} + 4;$

 

I-format

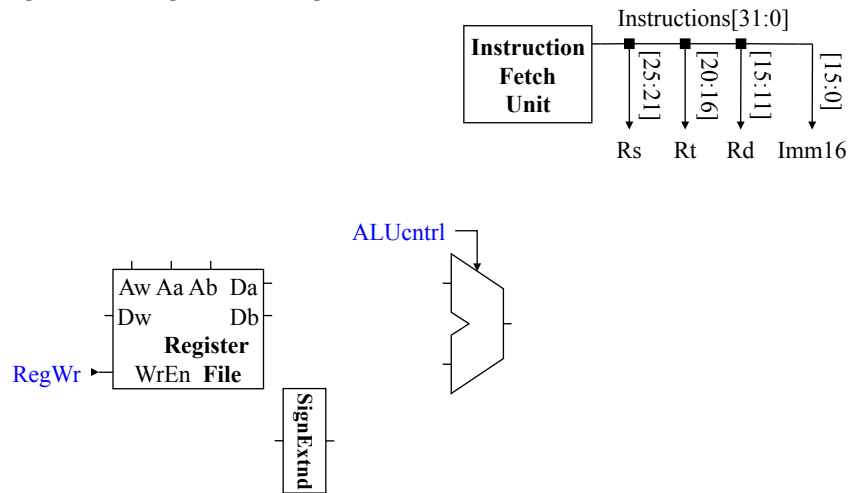
## Datapath + Immediate Ops

$\text{Reg}[\text{rt}] = \text{Reg}[\text{rs}] + \text{SignExtend}(\text{imm})$ ;


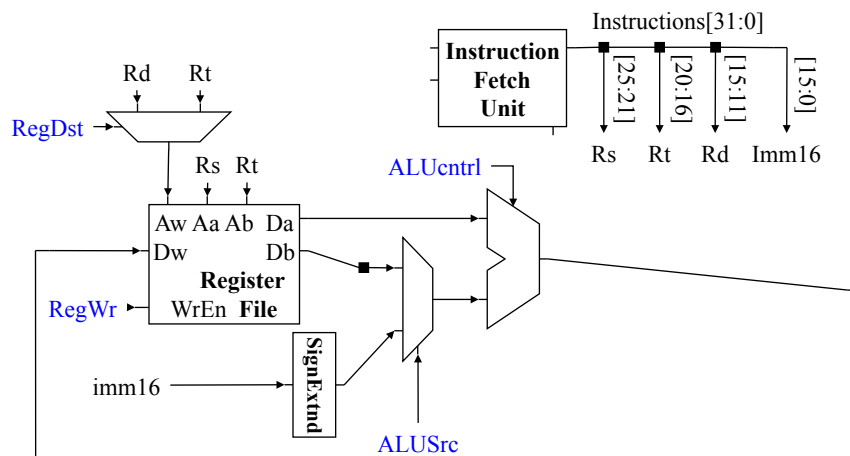
## Datapath + Immediate Ops


$\text{Reg}[\text{rt}] = \text{Reg}[\text{rs}] + \text{SignExtend}(\text{imm})$ ;


 
## Load RTL

**Load Instruction:** `lw rt, imm(rs)`


```
Instruction = Mem[PC];
Addr = Reg[rs] + SignExtend(imm);
Reg[rt] = Mem[Addr];
PC = PC + 4;
```



I-format
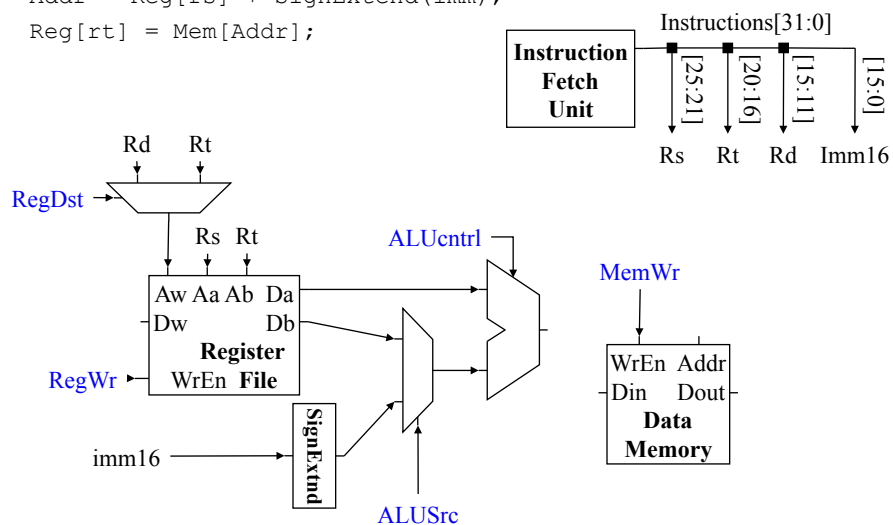
## Datapath + Load


```
Addr = Reg[rs] + SignExtend(imm);
Reg[rt] = Mem[Addr];
```




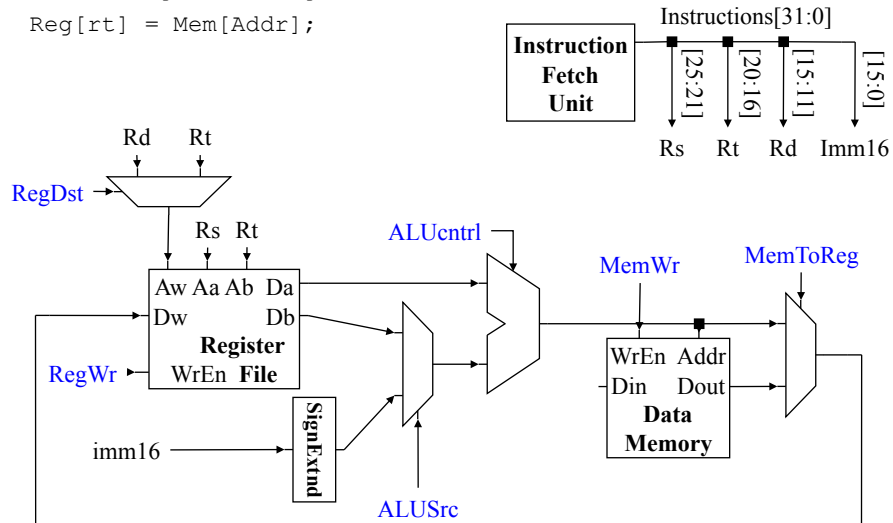
## Datapath + Load


```
Addr = Reg[rs] + SignExtend(imm);
Reg[rt] = Mem[Addr];
```



16
 
## Store RTL

```
Store Instruction: sw rt, imm(rs)
Instruction = Mem[PC];
Addr = Reg[rs] + SignExtend(imm);
Mem[Addr] = Reg[rt];
PC = PC + 4;
```




I-format

## Datapath + Store

$\text{Addr} = \text{Reg}[\text{rs}] + \text{SignExtend}(\text{imm});$

$\text{Mem}[\text{Addr}] = \text{Reg}[\text{rt}];$

Note: State of RegWr, MemToReg?

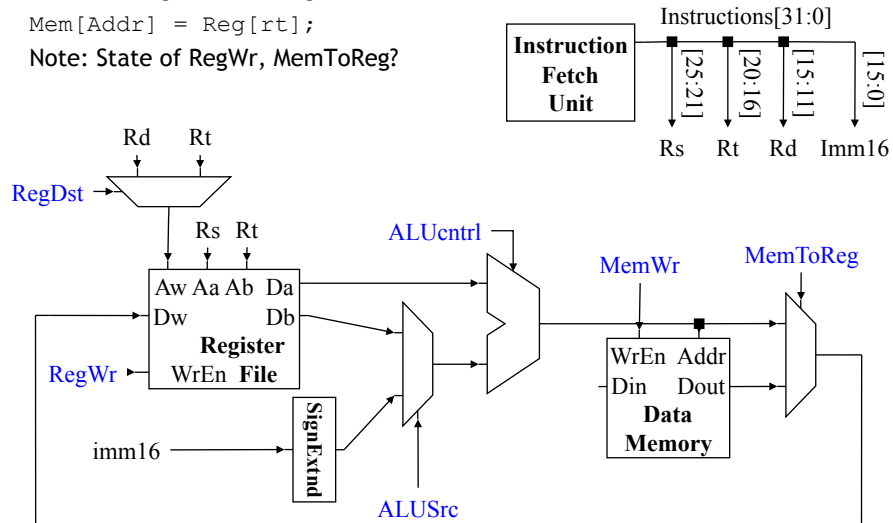


## Datapath + Store

$\text{Addr} = \text{Reg}[\text{rs}] + \text{SignExtend}(\text{imm});$

$\text{Mem}[\text{Addr}] = \text{Reg}[\text{rt}];$

RegWr false during stores.

MemToReg is Don't Care.

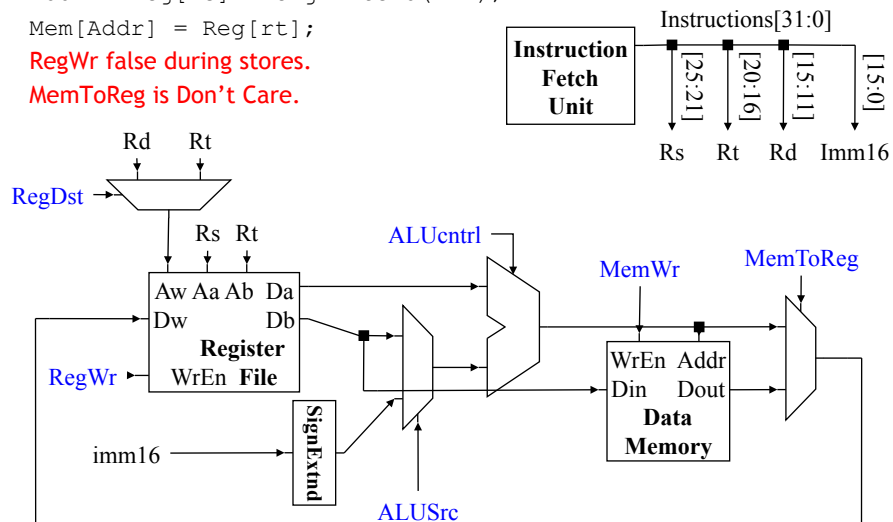


## Branch RTL

**Branch Instruction:** beq rs, rt, imm

```

 Instruction = Mem[PC];
Cond = (Reg[rs] - Reg[rt]) == 0;           // Test equality
if (Cond)
    PC = PC + 4 + (SignExtend(imm) * 4); // Neg for backward
    // *4: LBits == 00
else
    PC = PC + 4;
    
```




I-format
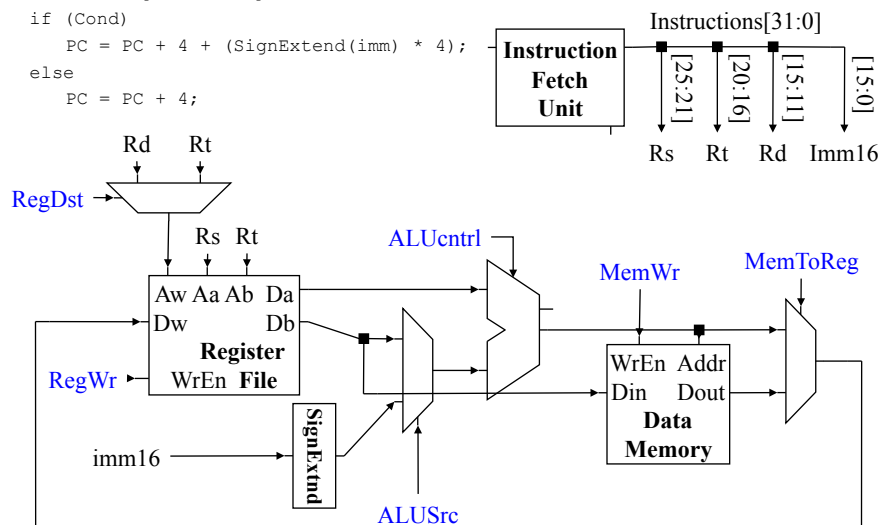
## Datapath + Branch

```

Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond)
    PC = PC + 4 + (SignExtend(imm) * 4);
else
    PC = PC + 4;
    
```




## Datapath + Branch

```

Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond)
    PC = PC + 4 + (SignExtend(imm) * 4);
else
    PC = PC + 4;

```

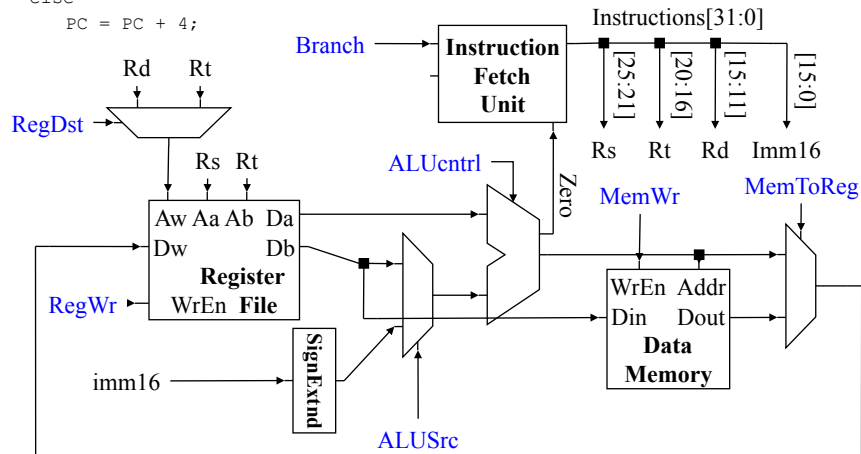


22

## Instruction Fetch + Branch

```

Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond)
    PC = PC + 4 + SignExtend(imm)*4;
else
    PC = PC + 4;

```

 


## Instruction Fetch + Branch

```

Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond)
    PC = PC + 4 + (SignExtend(imm) * 4);
else
    PC = PC + 4;

```

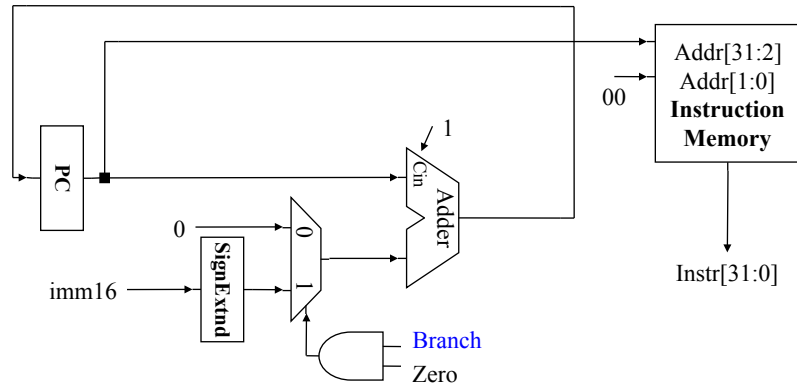


24

## Jump RTL

```

Store Instruction: j target
Instruction = Mem[PC];
PC = { PC[31:28], target[25:0], "00" };


```

 

J-format

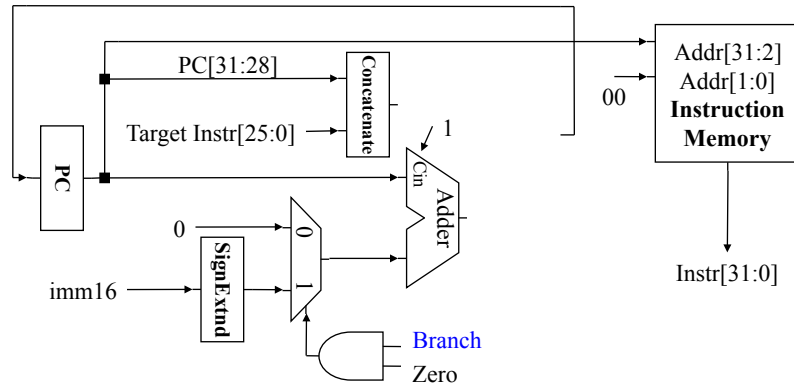
## Instruction Fetch + Jump

$PC = \{ PC[31:28], \text{target}[25:0], "00" \};$



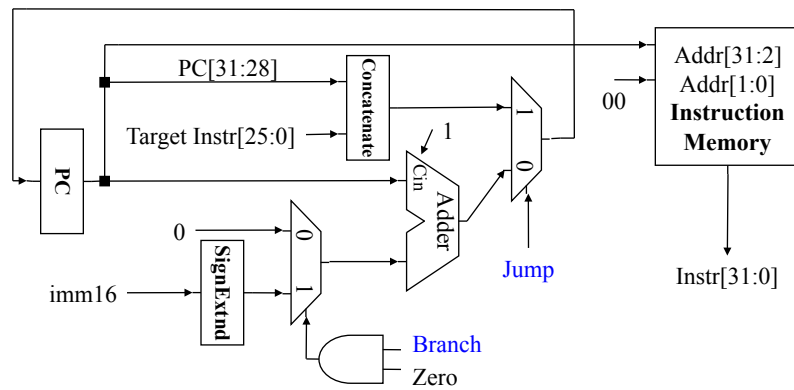
## Instruction Fetch + Jump


$PC = \{ PC[31:28], \text{target}[25:0], "00" \};$



## Complete Datapath

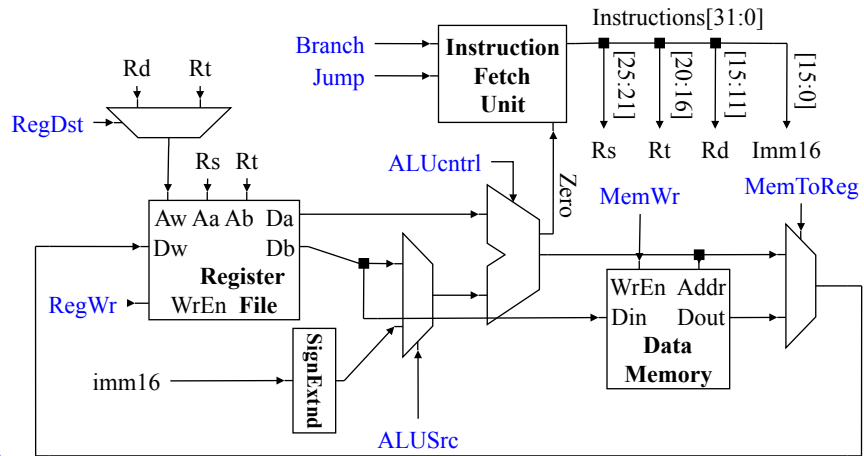

## Complete Fetch Unit

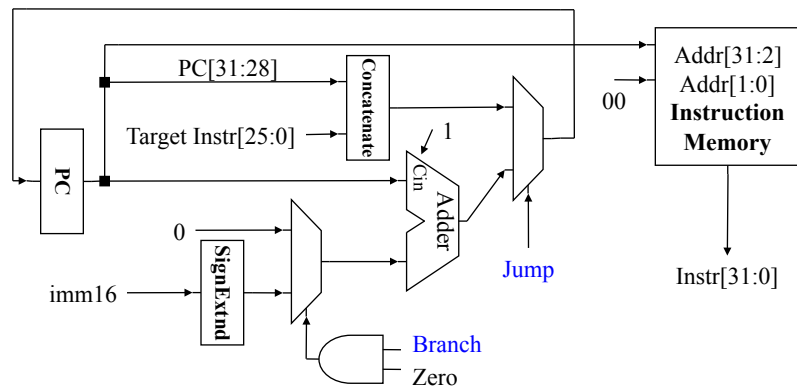


- Identify control points for pieces of datapath
  - Instruction Fetch Unit
  - ALU
  - Memories
  - Datapath muxes
  - Etc.
- Use RTL for determine per-instruction control assignments

[illegible]


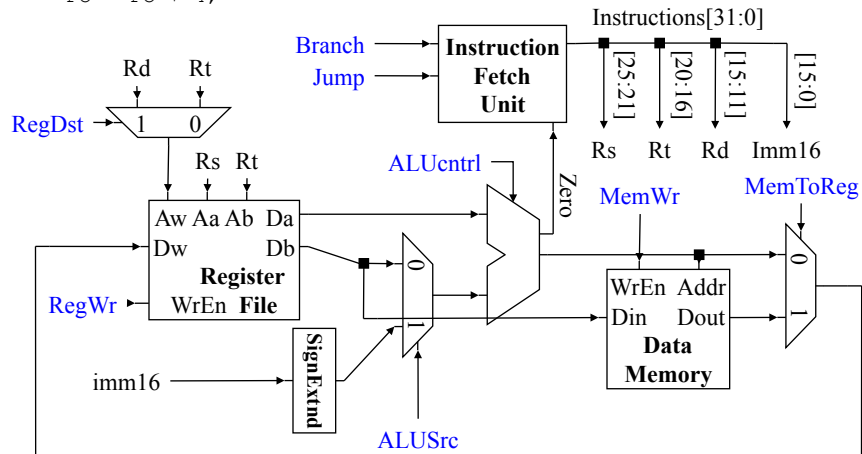
## Add Control

```
add rd, rs, rt
Instruction = Mem[PC];
Reg[rd] = Reg[rs] + Reg[rt];
PC = PC + 4;
```




## Control Signals

Func	100000	100010	XXXXXX	XXXXXX	XXXXXX	XXXXXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
RegDst	1					
ALUSrc	0					
MemToReg	0					
RegWr	1					
MemWr	0					
Branch	0					
Jump	0					
ALUCntrl	Add					
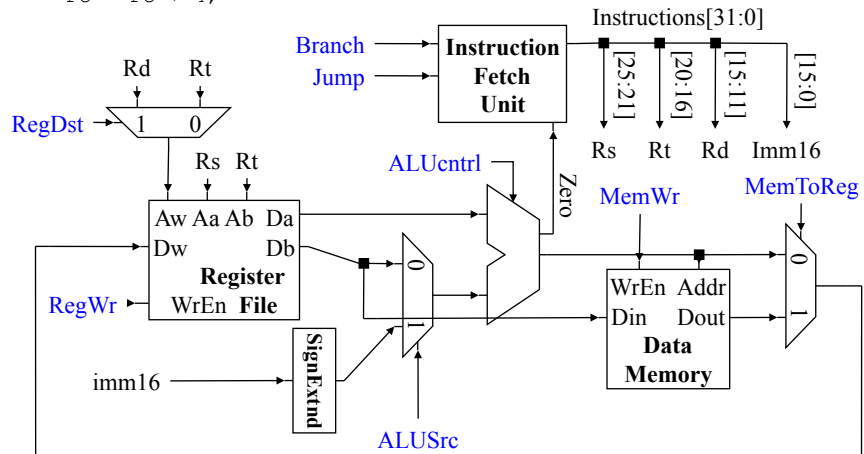
## Subtract Control

```
sub rd, rs, rt
Instruction = Mem[PC];
Reg[rd] = Reg[rs] - Reg[rt];
PC = PC + 4;
```




## Control Signals

Func	100000	100010	XXXXXX	XXXXXX	XXXXXX	XXXXXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
RegDst	1	1				
ALUSrc	0	0				
MemToReg	0	0				
RegWr	1	1				
MemWr	0	0				
Branch	0	0				
Jump	0	0				
ALUCntrl	Add	Sub				
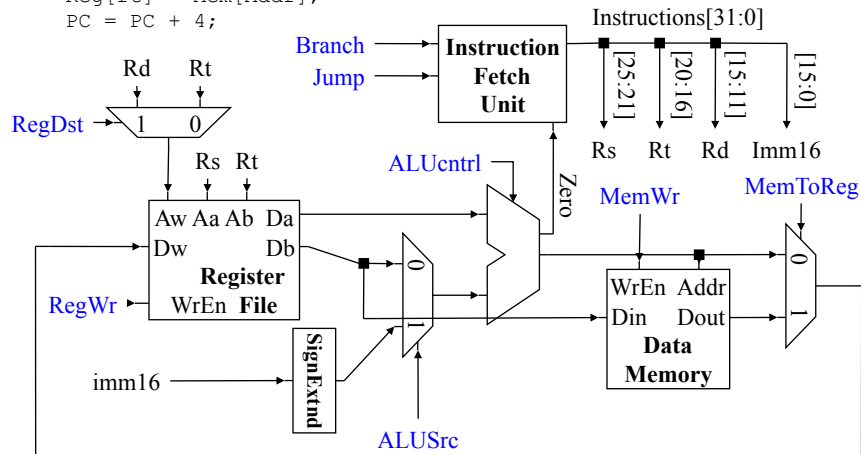
## Load Control

```
lw rt, imm(rs)
Instruction = Mem[PC];
Addr = Reg[rs] + SignExtend(imm);
Reg[rt] = Mem[Addr];
PC = PC + 4;
```




## Control Signals

Func	100000	100010	XXXXXX	XXXXXX	XXXXXX	XXXXXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
RegDst	1	1	0			
ALUSrc	0	0	1			
MemToReg	0	0	1			
RegWr	1	1	1			
MemWr	0	0	0			
Branch	0	0	0			
Jump	0	0	0			
ALUCntrl	Add	Sub	Add			
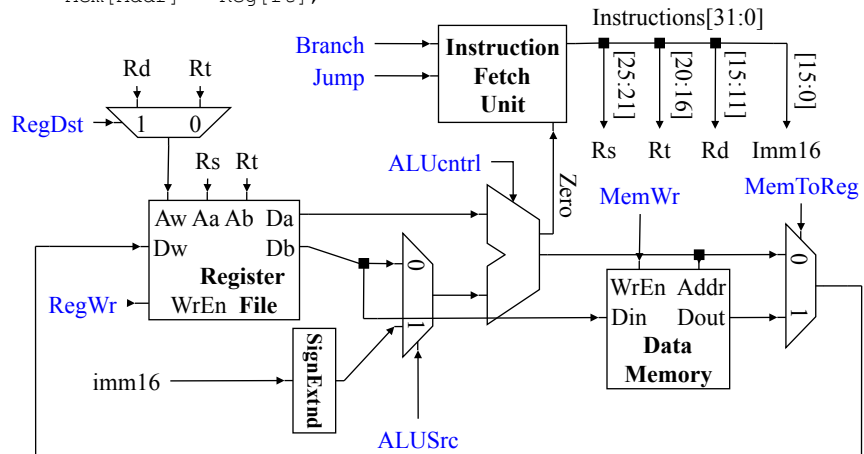
## Store Control

```
sw rt, imm(rs)
Instruction = Mem[PC];
Addr = Reg[rs] + SignExtend(imm);
Mem[Addr] = Reg[rt];
```



## Control Signals


Func	100000	100010	XXXXXX	XXXXXX	XXXXXX	XXXXXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
RegDst	1	1	0	X		
ALUSrc	0	0	1	1		
MemToReg	0	0	1	X		
RegWr	1	1	1	0		
MemWr	0	0	0	1		
Branch	0	0	0	0		
Jump	0	0	0	0		
ALUCntrl	Add	Sub	Add	Add		

## Branch Control

```

beq rs, rt, imm
Instruction = Mem[PC];
Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond) PC = PC+4+SignExtend(imm)*4;
else PC = PC + 4;

```

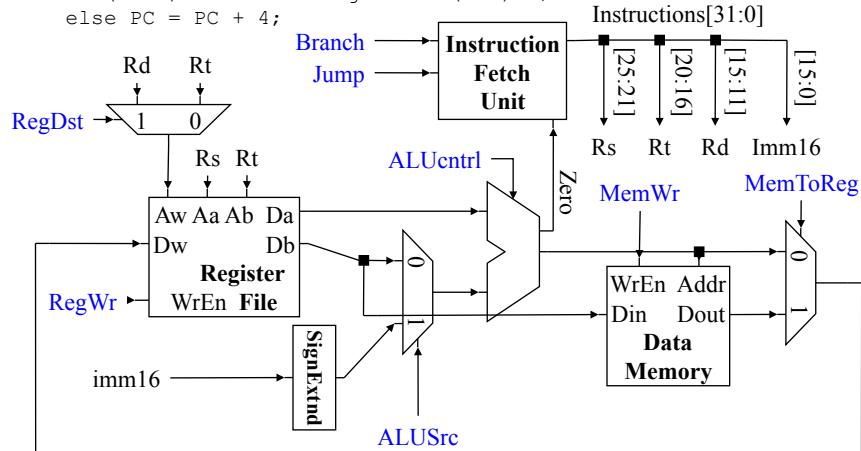


## Branch Control (cont.)

```

beq rs, rt, imm
Instruction = Mem[PC];
Cond = (Reg[rs] - Reg[rt]) == 0;
if (Cond) PC = PC+4+SignExtend(imm)*4;
else PC = PC + 4;

```

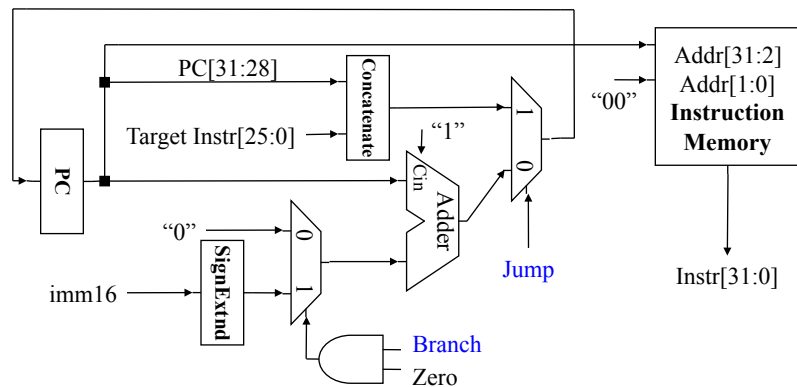

## Control Signals

Func	100000	100010	XXXXXX	XXXXXX	XXXXXX	XXXXXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	
RegDst	1	1	0	X	X	
ALUSrc	0	0	1	1	0	
MemToReg	0	0	1	X	X	
RegWr	1	1	1	0	0	
MemWr	0	0	0	1	0	
Branch	0	0	0	0	1	
Jump	0	0	0	0	0	
ALUCntrl	Add	Sub	Add	Add	Sub	


42

## Jump Control

```

j target
Instruction = Mem[PC];
PC = { PC[31:28], target[25:0], "00" };

```

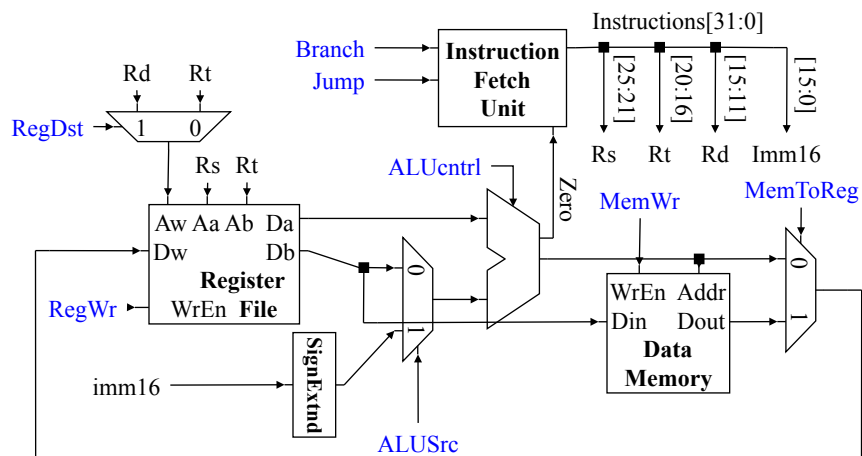


## Jump Control (cont.)

```

j target
Instruction = Mem[PC];
PC = { PC[31:28], target[25:0], "00" };

```

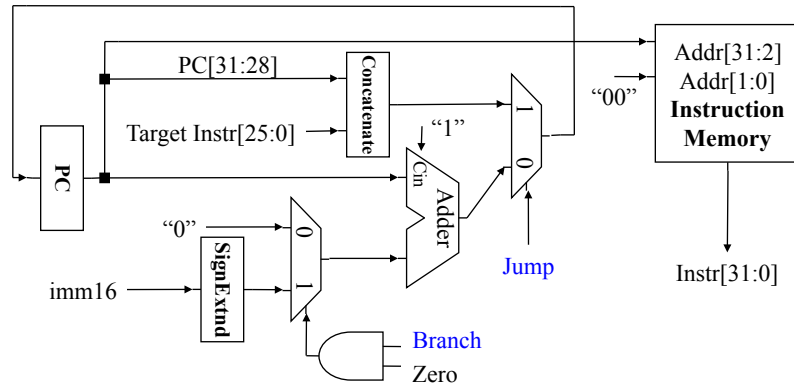

## Control Signals

Func	100000	100010	XXXXXX	XXXXXX	XXXXXX	XXXXXX
Op	000000	000000	100011	101011	000100	000010
	add	sub	lw	sw	beq	j
RegDst	1	1	0	X	X	X
ALUSrc	0	0	1	1	0	X
MemToReg	0	0	1	X	X	X
RegWr	1	1	1	0	0	0
MemWr	0	0	0	1	0	0
Branch	0	0	0	0	1	X
Jump	0	0	0	0	0	1
ALUCntrl	Add	Sub	Add	Add	Sub	X